

2.12
Solución

① PUNTO - EDO SISTEMA

Partiendo de:

$$L C \frac{d^2 V_c(t)}{dt^2} + R C \frac{dV_c(t)}{dt} + V_c(t) = V_i(t)$$

dividiendo por LC :

$$\frac{d^2 V_c(t)}{dt^2} + \frac{R}{L} \frac{dV_c(t)}{dt} + \frac{1}{LC} V_c(t) = \frac{1}{LC} V_i(t)$$

② PUNTO

• Partiendo de EDO:

$$L C \frac{d^2 V_c}{dt^2} + R C \frac{dV_c}{dt} + V_c(t) = V_i(t)$$

• Sabemos que: $V_R = R i(t)$ $V_L = L \frac{di(t)}{dt}$ $V_C = \frac{1}{C} \int i(t)$

$$V_i(t) = V_R + V_L + V_C$$

$$V_i(t) = R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t)$$

• Pasando los elementos al dominio de Laplace

$$R = R \quad L = LS \quad C = 1/s$$

A) Sea un circuito en serie, la corriente es la misma

$$V_i(s) = R I(s) + L s I(s) + \frac{1}{Cs} I(s)$$


$$V_i(s) = \left(R + L s + \frac{1}{Cs} \right) I(s)$$

$$H(s) = \frac{V_C}{V_i(s)} = \frac{\frac{1}{Cs} I(s)}{\left(R + L s + \frac{1}{Cs} \right) I(s)} = \frac{\frac{1}{Cs} (xCs)}{R + L s + \frac{1}{Cs} (xCs)}$$

$$H(s) = \frac{1}{RCs + Ls^2 + 1}$$

$$\rightarrow \boxed{H(s) = \frac{1}{Ls^2 + RCs + 1}}$$

2.12 Solución

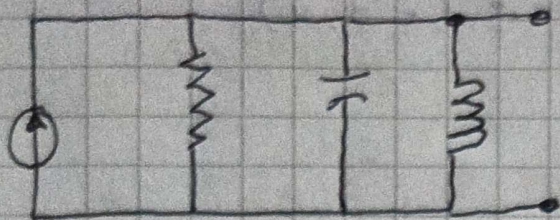

$$I_R(s) = \frac{V(s)}{R}$$

$$I_L(s) = V(s)$$

$$I_C(s) = V(s) \cdot Cs$$

Para condiciones iniciales cero, los elementos en el dominio de Laplace

$$R=R; \quad L=LS; \quad C=\frac{1}{Cs}$$

Aplicando ley de corrientes de Kirchhoff que dice que "la corriente total es la suma de las corrientes por cada rama".

$$I_{in}(s) = I_R(s) + I_L(s) + I_C(s)$$

$$I_{in}(s) = \frac{V(s)}{R} + \frac{V(s)}{LS} + V(s)Cs$$

$$I_{in}(s) = \left(\frac{1}{R} + \frac{1}{LS} + Cs \right) V(s)$$

$$H(s) = \frac{I_L(s)}{I_{in}(s)} = \frac{V(s)/LS}{\left(\frac{1}{R} + \frac{1}{LS} + Cs \right) V(s)}$$

$$= \frac{\frac{1}{LS}}{\left(\frac{1}{R} + \frac{1}{LS} + Cs \right)} \cdot \frac{x(Ls)}{x(Ls)}$$

$$H(s) = \frac{1}{\frac{L}{R}s + 1 + Lcs^2} = H(s) = \frac{1}{Lcs^2 + \frac{L}{R}s + 1}$$